



# William Stallings Computer Organization and Architecture 10<sup>th</sup> Edition



## Part One Overview

Chapter 1 organization, structure, architecture, function

Chapter 2 computer evolution and performance

## Part Two Computer System

Chapter 3 A top level-view of computer function and interconnection

Chapter 4 Cache memory

Chapter 5 Internal memory

Chapter 6 External memory

Chapter 7 Input/output

Chapter 8 Operating system support

## Part Three Arithmetic and Logic

Chapter 9 Number systems

Chapter 10 Computer arithmetic

Chapter 11 Digital logic

## Part Four The Central Processing Unit

Chapter 12 Instruction sets: Characteristics and functions

Chapter 13 Instruction sets: Addressing modes and formats

Chapter 14 Processor structure and function

Chapter 15 Reduced instruction set computers

Chapter 16 Instruction-level parallelism and superscalars processors

## Part Five Parallel Organization

Chapter 17 Parallel Processing


Chapter 18 Multicore computers

Chapter 19 Graphic Processing Unit

## Part Six Control Unit

Chapter 20 Control unit operation

Chapter 21 Microprogrammed control

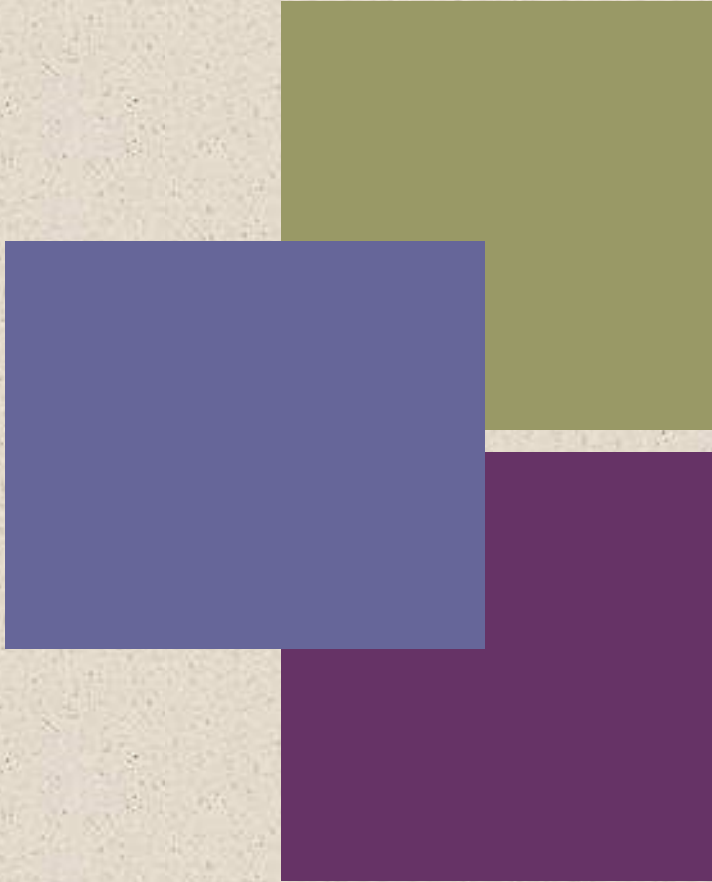

# + Chapter 11

## Digital Logic

# Boolean Algebra



- **Mathematical discipline** used to **design** and **analyze** the **behavior** of the digital circuitry in digital computers and other digital systems
- Named after George Boole
  - English mathematician
  - Proposed basic principles of the algebra in 1854
- Claude Shannon suggested Boolean algebra could be used to **solve problems** in **relay-switching circuit** design
- Is a **convenient** tool:
  - **Analysis**
    - It is an economical way of describing the function of digital circuitry
  - **Design**
    - Given a desired function, **Boolean algebra** can be applied to develop a simplified implementation of that function





# Boolean Variables and Operations

- Makes use of **variables** and **operations**
  - Are **logical**
  - A variable may take on the value **1** (**TRUE**) or **0** (**FALSE**)
  - Basic logical operations are **AND**, **OR**, and **NOT**
- **AND**
  - Yields **true** (**binary** value **1**) if and only if both of its **operands** are **true**
  - In the **absence** of **parentheses** the **AND** operation takes **precedence** over the **OR** operation
  - When no ambiguity will occur the **AND** operation is represented by simple **concatenation** instead of the **dot operator**
- **OR**
  - Yields true if either or both of its operands are true
- **NOT**
  - Inverts the value of its operand

# Table 11.1 Boolean Operators



(a) Boolean Operators of Two Input Variables

P	Q	NOT P ( $\bar{P}$ )	P AND Q ( $P \cdot Q$ )	P OR Q ( $P + Q$ )	P NAND Q ( $\overline{P \cdot Q}$ )	P NOR Q ( $\overline{P + Q}$ )	P XOR Q ( $P \oplus Q$ )
0	0	1	0	0	1	1	0
0	1	1	0	1	1	0	1
1	0	0	0	1	1	0	1
1	1	0	1	1	0	0	0

(b) Boolean Operators Extended to More than Two Inputs (A, B, ...)

Operation	Expression	Output = 1 if
AND	$A \cdot B \cdot \dots$	All of the set {A, B, ...} are 1.
OR	$A + B + \dots$	Any of the set {A, B, ...} are 1.
NAND	$\overline{A \cdot B \cdot \dots}$	Any of the set {A, B, ...} are 0.
NOR	$\overline{A + B + \dots}$	All of the set {A, B, ...} are 0.
XOR	$A \oplus B \oplus \dots$	The set {A, B, ...} contains an odd number of ones.



# Table 11.2







## Basic Identities of Boolean Algebra

### Basic Postulates

$A \cdot B = B \cdot A$	$A + B = B + A$	Commutative Laws
$A \cdot (B + C) = (A \cdot B) + (A \cdot C)$	$A + (B \cdot C) = (A + B) \cdot (A + C)$	Distributive Laws
$1 \cdot A = A$	$0 + A = A$	Identity Elements
$A \cdot \bar{A} = 0$	$A + \bar{A} = 1$	Inverse Elements




### Other Identities

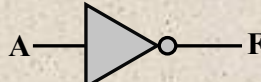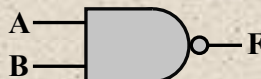$0 \cdot A = 0$	$1 + A = 1$	
$A \cdot A = A$	$A + A = A$	
$A \cdot (B \cdot C) = (A \cdot B) \cdot C$	$A + (B + C) = (A + B) + C$	Associative Laws
$\overline{A \cdot B} = \bar{A} + \bar{B}$	$\overline{A + B} = \bar{A} \cdot \bar{B}$	DeMorgan's Theorem




Name	Graphical Symbol	Algebraic Function	Truth Table															
AND		$F = A \bullet B$ or $F = AB$	<table><tr><th>A</th><th>B</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	F	0	0	0	0	1	0	1	0	0	1	1	1
A	B	F																
0	0	0																
0	1	0																
1	0	0																
1	1	1																
OR		$F = A + B$	<table><tr><th>A</th><th>B</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	F	0	0	0	0	1	1	1	0	1	1	1	1
A	B	F																
0	0	0																
0	1	1																
1	0	1																
1	1	1																
NOT		$F = \overline{A}$ or $F = A'$	<table><tr><th>A</th><th>F</th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	A	F	0	1	1	0									
A	F																	
0	1																	
1	0																	
NAND		$F = \overline{AB}$	<table><tr><th>A</th><th>B</th><th>F</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	F	0	0	1	0	1	1	1	0	1	1	1	0
A	B	F																
0	0	1																
0	1	1																
1	0	1																
1	1	0																
NOR		$F = \overline{A + B}$	<table><tr><th>A</th><th>B</th><th>F</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	F	0	0	1	0	1	0	1	0	0	1	1	0
A	B	F																
0	0	1																
0	1	0																
1	0	0																
1	1	0																
XOR		$F = A \oplus B$	<table><tr><th>A</th><th>B</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	F	0	0	0	0	1	1	1	0	1	1	1	0
A	B	F																
0	0	0																
0	1	1																
1	0	1																
1	1	0																

**Figure 11.1 Basic Logic Gates**



   

**Figure 11.2 Some Uses of NAND Gates**

   

**Figure 11.3 Some Uses of NOR Gates**

# Combinational Circuit

An interconnected set of **gates** whose output at any time is a **function** only of the input at that time

The appearance of the input is followed almost immediately by the appearance of the output, with only **gate delays**

Consists of  $n$  binary inputs and  $m$  binary outputs


Can be defined in three ways:

- **Truth table**
  - For each of the  $2^n$  possible combinations of input signals, the **binary** value of each of the  **$m$  output** signals is listed
- **Graphical symbols**
  - The interconnected layout of gates is depicted
- **Boolean equations**
  - Each output signal is expressed as a Boolean function of its input signals




**Table 11.3**  
**A Boolean Function of Three Variables**
  
<b>A</b>	<b>B</b>	<b>C</b>	<b>F</b>
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

 


**Figure 11.4 Sum-of-Products Implementation of Table 11.3**

 





**Figure 11.5 Product-of-Sums Implementation of Table 11.3**




**Figure 11.6 Simplified Implementation of Table 11.3**




**Figure 11.7 The Use of Karnaugh Maps to Represent Boolean Functions**

 


(a)  $\bar{A}BD$

 


(b)  $\bar{B}\bar{C}D$

 


(c)  $\bar{A}B\bar{D}$

 


(d)  $\bar{A}\bar{B}$

 


(e)  $B\bar{C}$

 


(f)  $B\bar{D}$

 

(g)  $\bar{A}$

 

(h)  $\bar{D}$

 

(i)  $C$

## Karnaugh Maps

**BC**

		00	01	11	10
<b>A</b> 0				1	1
1					1

(a)  $F = \bar{A}B + B\bar{C}$

**CD**

		00	01	11	10
<b>AB</b> 00					
01			1		
11			1	1	
10				1	

(b)  $F = \bar{B}\bar{C}D + ACD$

**Figure 11.9 Overlapping Groups**



# Table 11.4

## Truth Table for the One-Digit Packed Decimal Incrementer

Input					Output				
Number	A	B	C	D	Number	W	X	Y	Z
0	0	0	0	0	1	0	0	0	1
1	0	0	0	1	2	0	0	1	0
2	0	0	1	0	3	0	0	1	1
3	0	0	1	1	4	0	1	0	0
4	0	1	0	0	5	0	1	0	1
5	0	1	0	1	6	0	1	1	0
6	0	1	1	0	7	0	1	1	1
7	0	1	1	1	8	1	0	0	0
8	1	0	0	0	9	1	0	0	1
9	1	0	0	1	0	0	0	0	0
Don't care con- dition	1	0	1	0		d	d	d	d
	1	0	1	1		d	d	d	d
	1	1	0	0		d	d	d	d
	1	1	0	1		d	d	d	d
	1	1	1	0		d	d	d	d
	1	1	1	1		d	d	d	d

Table 11.4 Truth Table for the One-Digit Packed Decimal Incrementer

	CD			
	00	01	11	10
AB	00			
	01		1	
	11	d	d	d
	10	1		d

(a)  $W = A\bar{D} + \bar{A}BCD$

	CD			
	00	01	11	10
AB	00		1	
	01	1	1	1
	11	d	d	d
	10		d	d

(b)  $X = B\bar{D} + B\bar{C} + BCD$

	CD			
	00	01	11	10
AB	00		1	1
	01		1	
	11	d	d	d
	10		d	d

(c)  $Y = \bar{A}\bar{C}D + \bar{A}C\bar{D}$

	CD			
	00	01	11	10
AB	00	1		1
	01	1		1
	11	d	d	d
	10	1	d	d

(d)  $Z = \bar{D}$

**Figure 11.10 Karnaugh Maps for the Incrementer**



## Table 11.5

### First Stage of Quine-McCluskey Method

(for  $F = ABCD + AB\bar{D} + A\bar{B} + A\bar{C}D + BCD + BC\bar{D} + B\bar{D} + D$ )

Product Term	Index	A	B	C	D	
$\bar{A}\bar{B}\bar{C}D$	1	0	0	0	1	✓
$\bar{A}B\bar{C}D$	5	0	1	0	1	✓
$\bar{A}BC\bar{D}$	6	0	1	1	0	✓
$AB\bar{C}\bar{D}$	12	1	1	0	0	✓
$\bar{A}BCD$	7	0	1	1	1	✓
$A\bar{B}CD$	11	1	0	1	1	✓
$AB\bar{C}D$	13	1	1	0	1	✓
$ABCD$	15	1	1	1	1	✓




# Table 11.6

## Last Stage of Quine-McCluskey Method


(for  $F = ABCD + AB\bar{D} + A\bar{B}C + A\bar{B}\bar{C}D + B\bar{C}D + B\bar{C}\bar{D} + B\bar{C}D + D$ )

	$ABCD$	$AB\bar{C}D$	$AB\bar{C}\bar{D}$	$A\bar{B}CD$	$\bar{A}BCD$	$\bar{A}BC\bar{D}$	$\bar{A}\bar{B}CD$	$\square\square\square D$
$BD$	X	X			X		X	
$\bar{A}\bar{C}D$							<span style="border: 1px solid black;">X</span>	$\ddot{A}$
$\bar{A}BC$					<span style="border: 1px solid black;">X</span>	$\ddot{A}$		
$AB\bar{C}$		<span style="border: 1px solid black;">X</span>	$\ddot{A}$					
$ACD$	<span style="border: 1px solid black;">X</span>			$\ddot{A}$				

 

**Figure 11.11 NAND Implementation of Table 11.3**

 

 


**Figure 11.12 4-to-1 Multiplexer Representation**

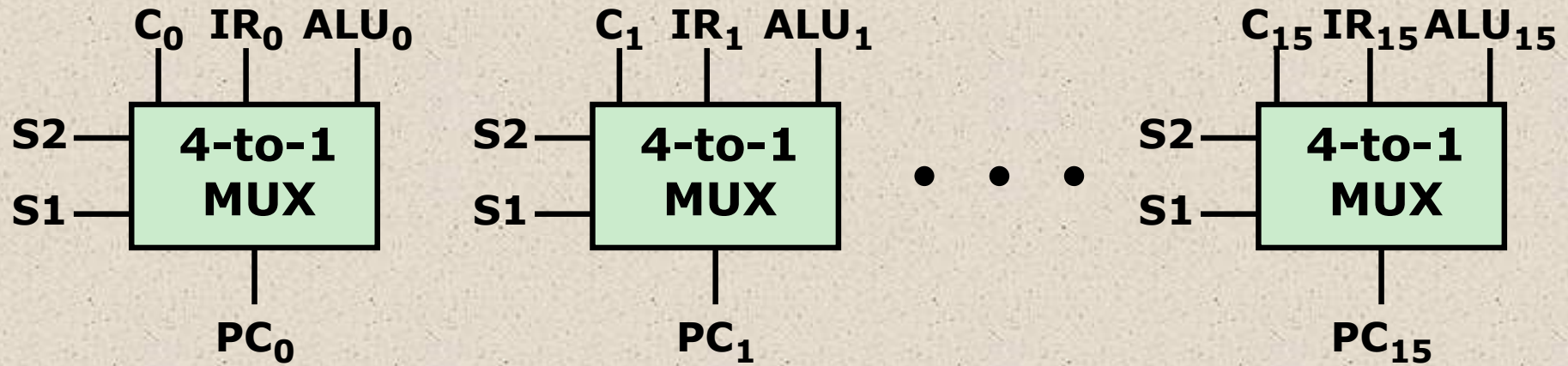


**Table 11.7**  
**4-to-1 Multiplexer Truth Table**

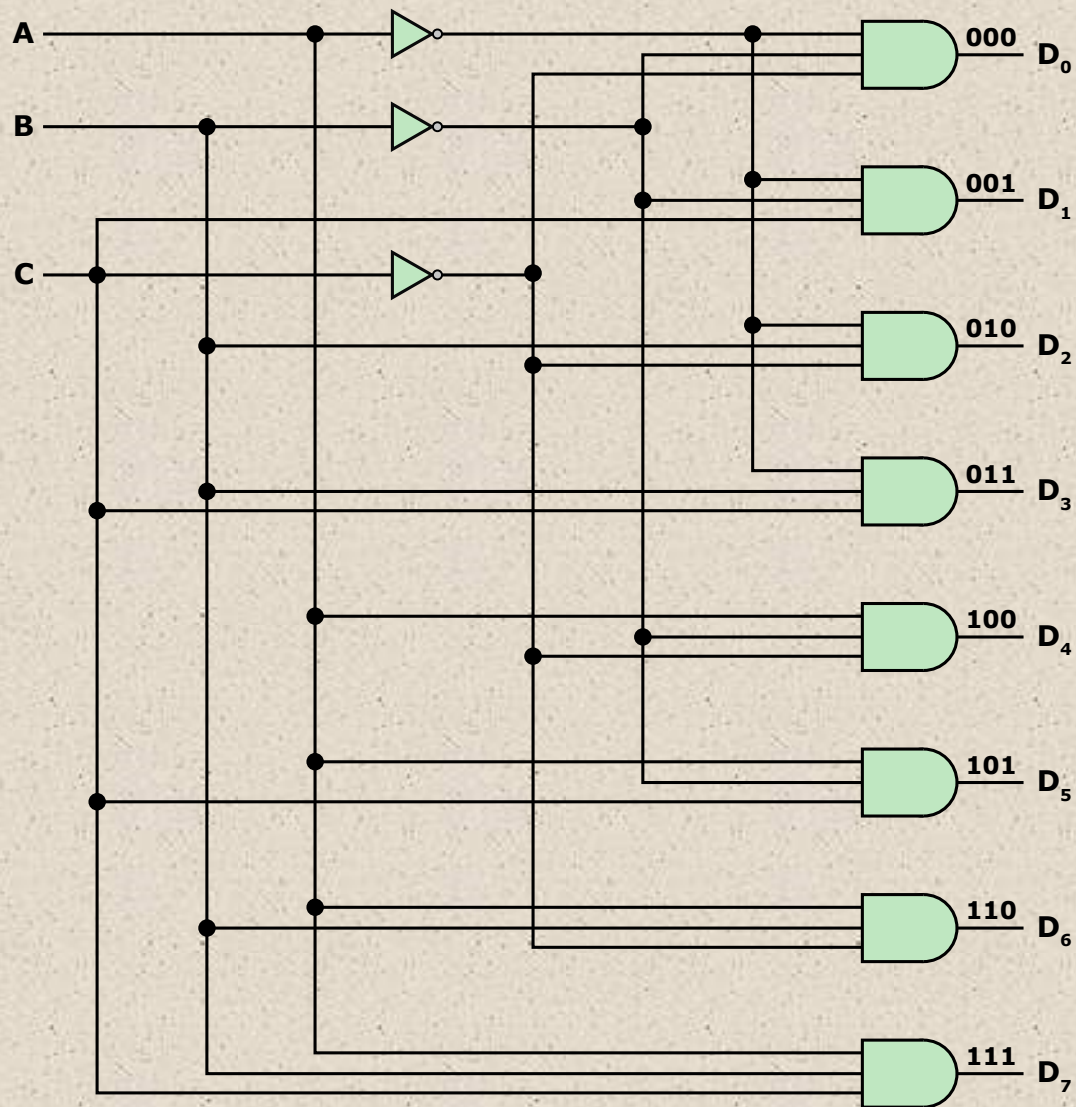
S2	S1	F
0	0	D0
0	1	D1
1	0	D2
1	1	D3



**Figure 11.13 Multiplexer Implementation**

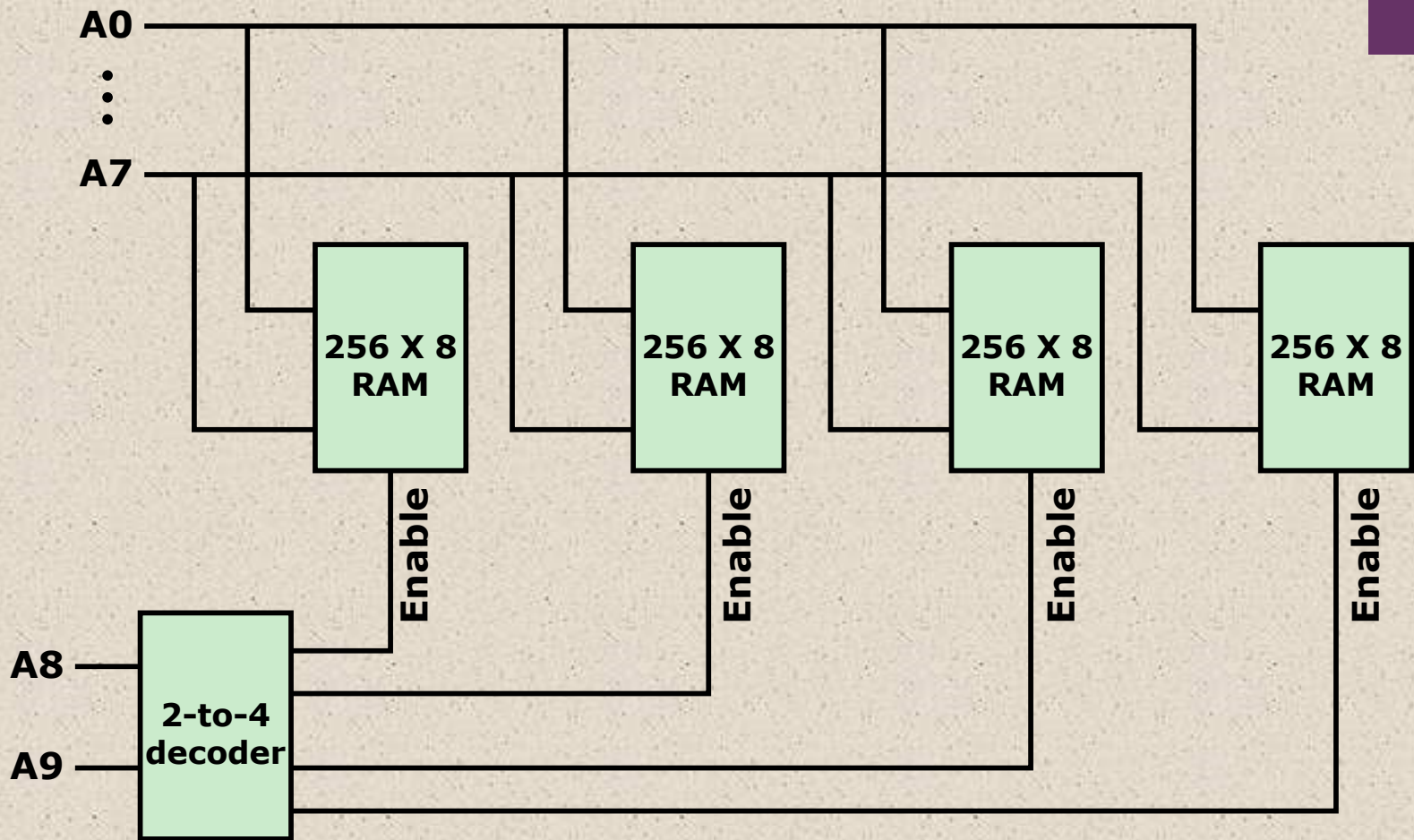


**Figure 11.14 Multiplexer Input to Program Counter**




**Figure 11.15 Decoder with 3 Inputs and  $2^3 = 8$  Outputs**





**Figure 11.16 Address Decoding**

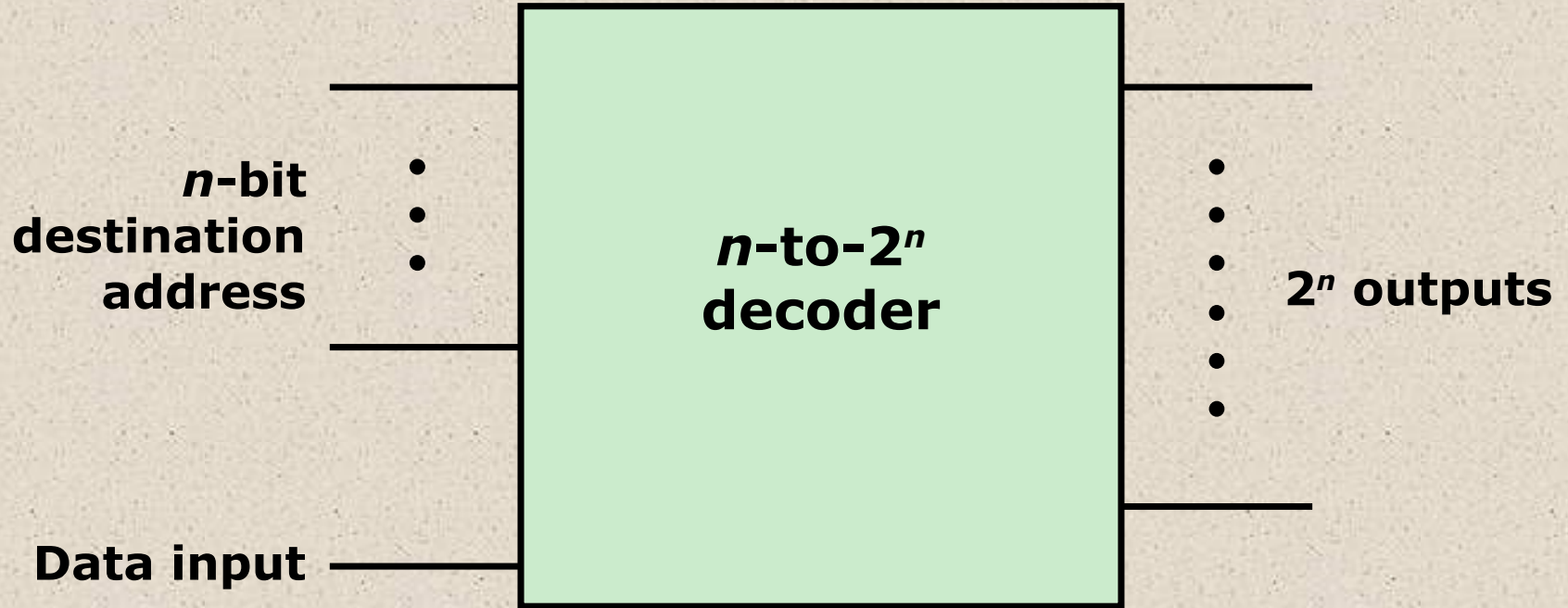

**Figure 11.17 Implementation of a Demultiplexer Using a Decoder**

# Read-Only Memory (ROM)




- Memory that is implemented with **combinational** circuits
  - Combinational circuits are often referred to as “memoryless” circuits because their output depends only on their current input and no history of prior inputs is retained
- Memory unit that performs only the **read** operation
  - Binary information stored in a ROM is **permanent** and is created during the **fabrication** process
  - A given input to the ROM (address lines) always produces the same output (data lines)
  - Because the outputs are a function only of the present inputs, ROM is a combinational circuit

# Table 11.8

## Truth Table for a ROM

Input				Output			
$X_1$	$X_2$	$X_3$	$X_4$	$Z_1$	$Z_2$	$Z_3$	$Z_4$
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	0	1	0	1	1	1
0	1	1	0	0	1	0	1
0	1	1	1	0	1	0	0
1	0	0	0	1	1	0	0
1	0	0	1	1	1	0	1
1	0	1	0	1	1	1	1
1	0	1	1	1	1	1	0
1	1	0	0	1	0	1	0
1	1	0	1	1	0	1	1
1	1	1	0	1	0	0	1
1	1	1	1	1	0	0	0

 

**Figure 11.18 A 64-Bit ROM**





# Table 11.9


## Binary Addition Truth Tables

(a) Single-Bit Addition


A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

(b) Addition with Carry Input


$C_{in}$	A	B	Sum	$C_{out}$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

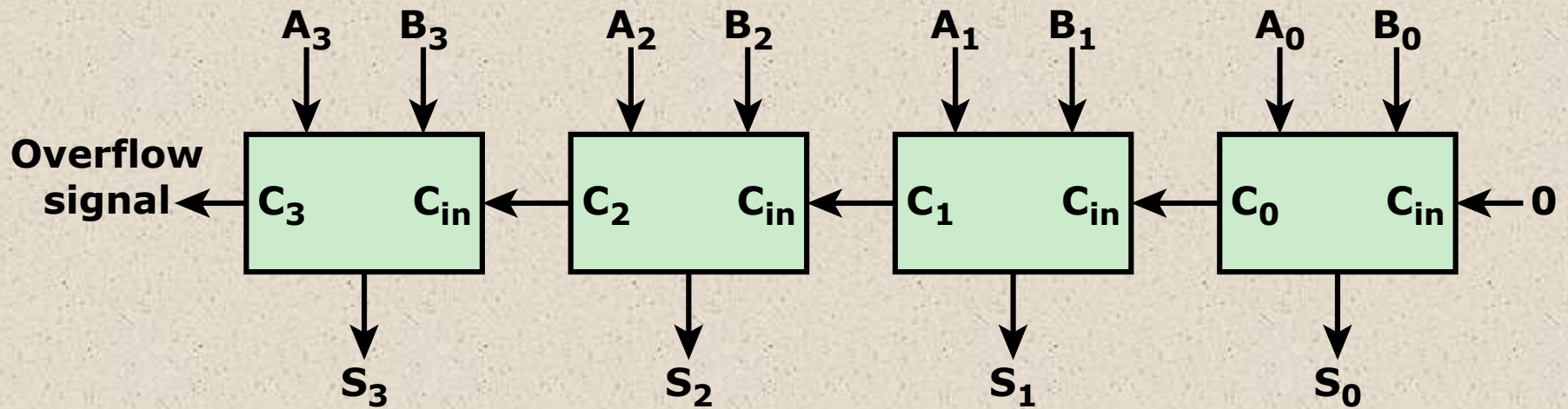

**Figure 11.19 4-Bit Adder**

 


**Figure 11.20 Implementation of an Adder**

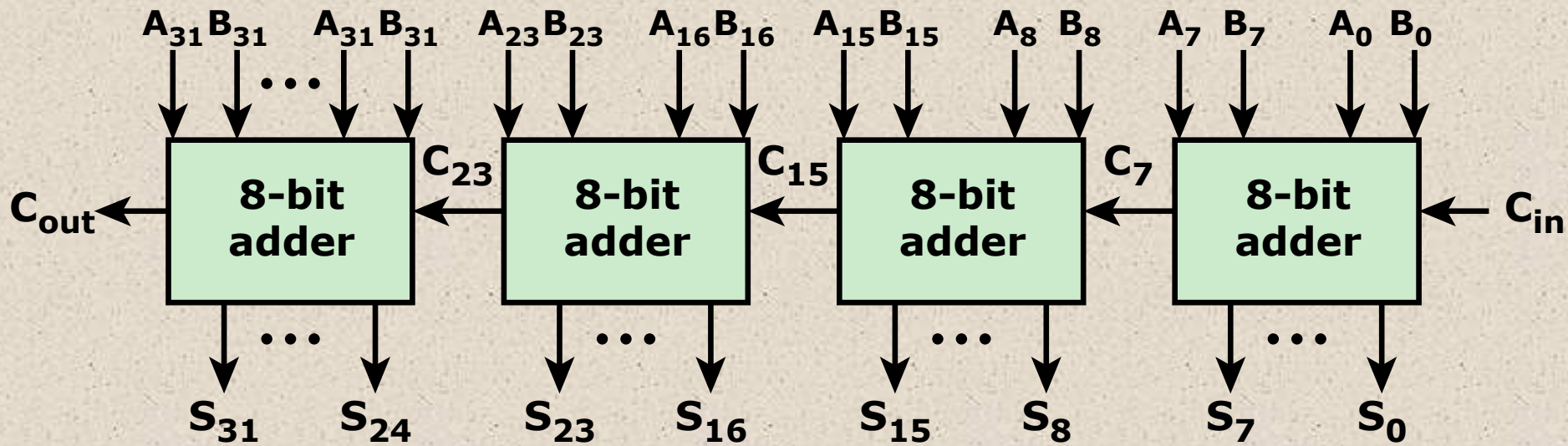

**Figure 11.21 Construction of a 32-Bit Adder Using 8-Bit Adders**

# Sequential Circuit

Sequential  
Circuit

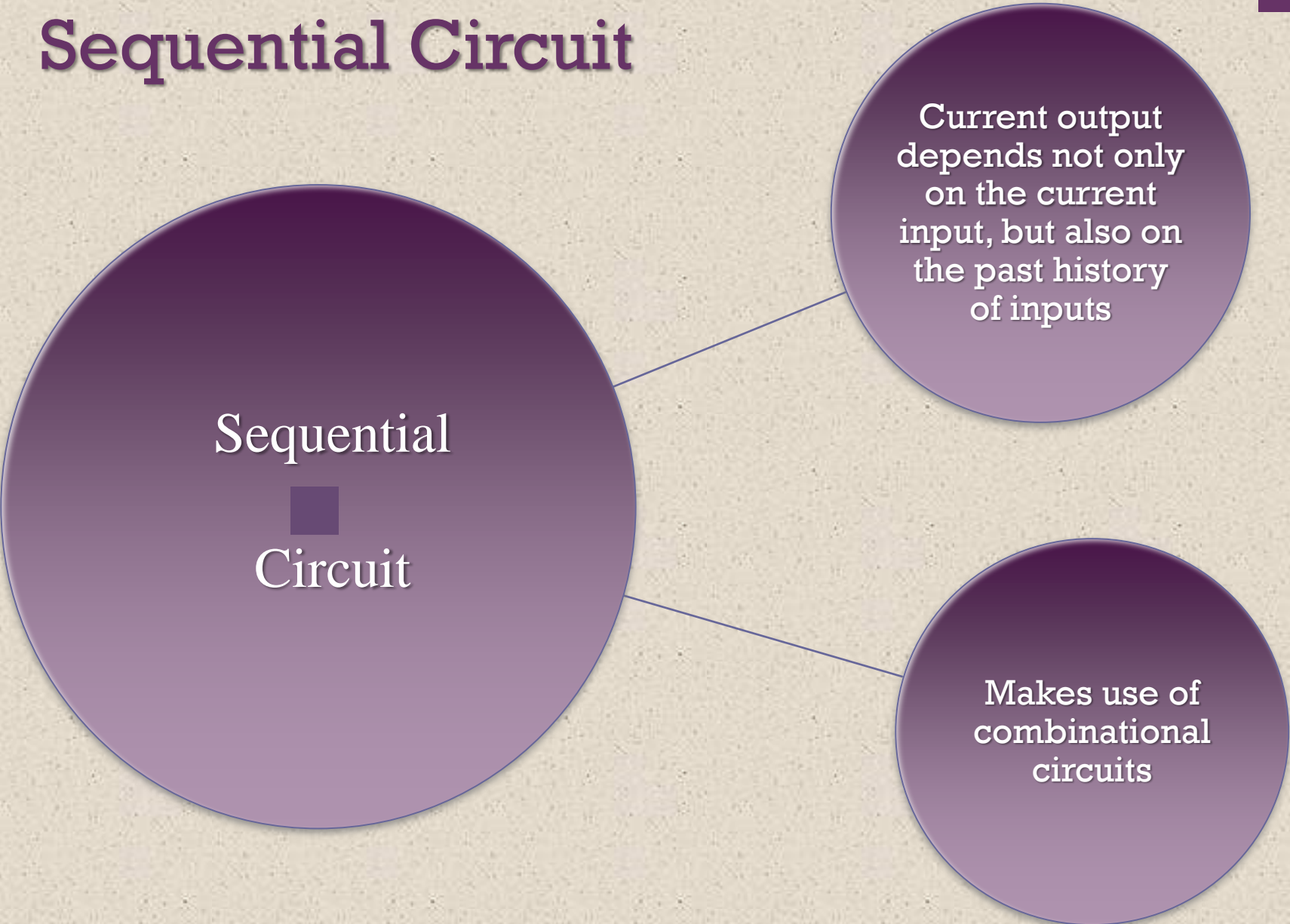

```
graph TD; A((Sequential Circuit)) --- B((Current output depends not only on the current input, but also on the past history of inputs)); A --- C((Makes use of combinational circuits))
```

Current output depends not only on the current input, but also on the past history of inputs

Makes use of combinational circuits







# Flip-Flops



- Simplest form of sequential circuit
- There are a variety of flip-flops, all of which share two properties:
  1. The flip-flop is a bistable device. It exists in one of two states and, in the absence of input, remains in that state. Thus, the flip-flop can function as a 1-bit memory.
  2. The flip-flop has two outputs, which are always the complements of each other.

 

**Figure 11.22 The S-R Latch Implemented with NOR Gates**

 

**Figure 11.23 NOR S-R Latch Timing Diagram**

# Table 11.10 The S-R Latch



(a) Characteristic Table


Current Inputs SR	Current State $Q_n$	Next State $Q_{n+1}$
00	0	0
00	1	1
01	0	0
01	1	0
10	0	1
10	1	1
11	0	—
11	1	—

(b) Simplified Characteristic Table

S	R	$Q_{n+1}$
0	0	$Q_n$
0	1	0
1	0	1
1	1	—

(c) Response to Series of Inputs


$t$	0	1	2	3	4	5	6	7	8	9
S	1	0	0	0	0	0	0	0	1	0
R	0	0	0	1	0	0	1	0	0	0
$Q_{n+1}$	1	1	1	0	0	0	0	0	1	1

 

Asynchronous operation for dealing time delay


**Figure 11.24 Clocked S-R Flip Flop**



 

Data flip-flop (RAM; time delay)




**Figure 11.25 D Flip Flop**

 

Gate implementation


**Figure 11.26 J-K Flip Flop**

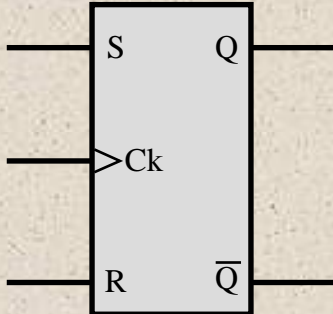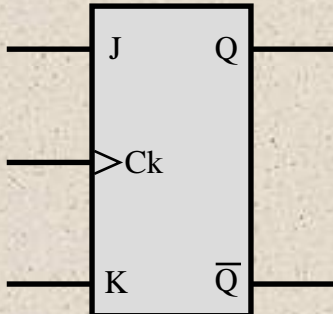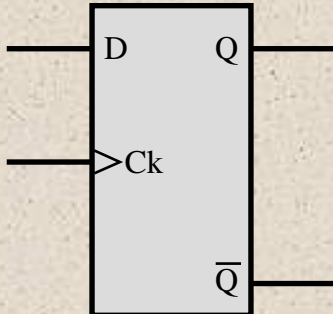

Name	Graphical Symbol	Truth Table															
S-R		<table><tr><th>S</th><th>R</th><th><math>Q_{n+1}</math></th></tr><tr><td>0</td><td>0</td><td><math>Q_n</math></td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>—</td></tr></table>	S	R	$Q_{n+1}$	0	0	$Q_n$	0	1	0	1	0	1	1	1	—
S	R	$Q_{n+1}$															
0	0	$Q_n$															
0	1	0															
1	0	1															
1	1	—															
J-K		<table><tr><th>J</th><th>K</th><th><math>Q_{n+1}</math></th></tr><tr><td>0</td><td>0</td><td><math>Q_n</math></td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td><math>\overline{Q_n}</math></td></tr></table>	J	K	$Q_{n+1}$	0	0	$Q_n$	0	1	0	1	0	1	1	1	$\overline{Q_n}$
J	K	$Q_{n+1}$															
0	0	$Q_n$															
0	1	0															
1	0	1															
1	1	$\overline{Q_n}$															
D		<table><tr><th>D</th><th><math>Q_{n+1}</math></th></tr><tr><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td></tr></table>	D	$Q_{n+1}$	0	0	1	1									
D	$Q_{n+1}$																
0	0																
1	1																


Basic Flip-Flops

# A set of 1-bit memories

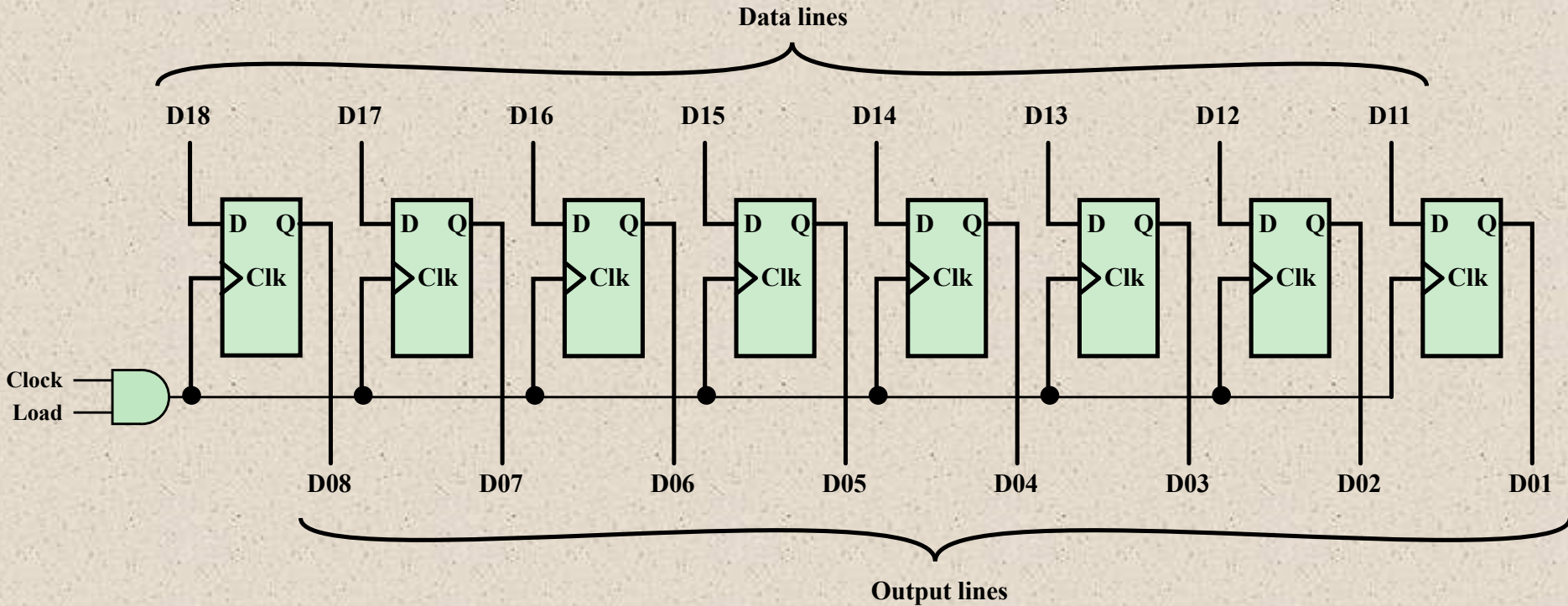

Output of multiplexers

**Figure 11.28 8-Bit Parallel Register**

 

**Figure 11.29 5-Bit Shift Register**


Interface to serial I/O devices; Logical shift; Rotate functions



# Counter

- A register whose value is easily incremented by 1 **modulo** the **capacity** of the **register**
- After the maximum value is achieved the next increment sets the **counter value** to 0
- An example of a counter in the CPU is the program counter
- Can be designated as:
  - **Asynchronous**
    - Relatively slow because the output of one flip-flop triggers a change in the status of the next flip-flop
  - **Synchronous**
    - All of the **flip-flops change state** at the same time
    - Because it is faster it is the kind used in CPUs

# Ripple counter

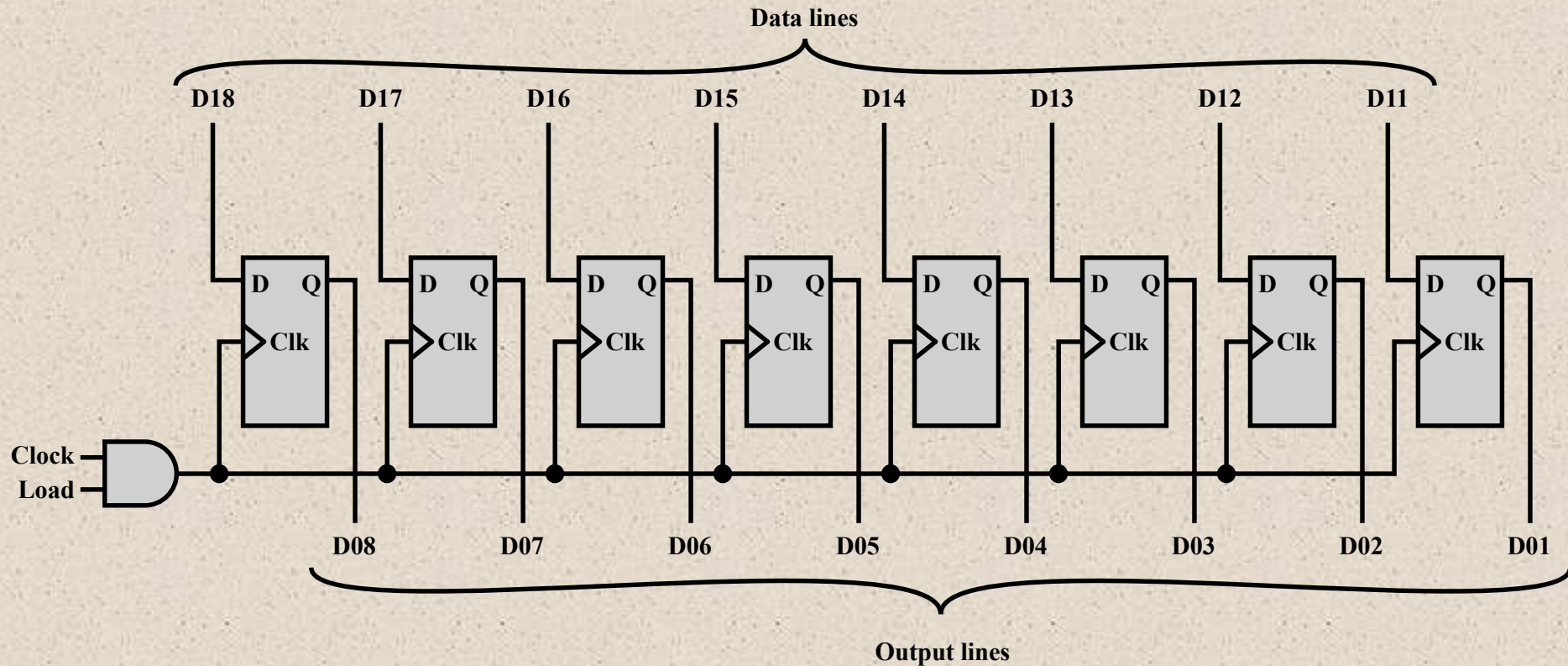

**Figure 11.30 8-Bit Parallel Register**



(a) Truth table

C	B	A	Jc	Kc	Jb	Kb	Ja	Ka
0	0	0	0	d	0	d	1	d
0	0	1	0	d	1	d	d	1
0	1	0	0	d	d	0	1	d
0	1	1	1	d	d	1	d	1
1	0	0	d	0	0	d	1	d
1	0	1	d	0	1	d	d	1
1	1	0	d	0	d	0	1	d
1	1	1	d	1	d	1	d	1

(b) Karnaugh maps

Jc = BA

		BA			
		00	01	11	10
C	0			1	
	1	d	d	d	d

Kc = BA

		BA			
		00	01	11	10
C	0	d	d	d	d
	1			1	

Jb = A

		BA			
		00	01	11	10
C	0		1	d	d
	1		1	d	d

Kb = A

		BA			
		00	01	11	10
C	0	d	d	1	
	1	d	d	1	


Ja = 1

		BA			
		00	01	11	10
C	0	1	d	d	1
	1	1	d	d	1

Ka = 1

		BA			
		00	01	11	10
C	0	d	1	1	d
	1	d	1	1	d

(c) Logic diagram

 

## Design of a Synchronous Counter

## **Programmable Logic Device (PLD)**

A general term that refers to any type of integrated circuit used for implementing digital hardware, where the chip can be configured by the end user to realize different designs. Programming of such a device often involves placing the chip into a special programming unit, but some chips can also be configured “in-system”. Also referred to as a field-programmable device (FPD).

## **Programmable Logic Array (PLA)**

A relatively small PLD that contains two levels of logic, an AND-plane and an OR-plane, where both levels are programmable.

## **Programmable Array Logic (PAL)**

A relatively small PLD that has a programmable AND-plane followed by a fixed OR-plane.

## **Simple PLD (SPLD)**

A PLA or PAL.

## **Complex PLD (CPLD)**

A more complex PLD that consists of an arrangement of multiple SPLD-like blocks on a single chip.

## **Field-Programmable Gate Array (FPGA)**

✚ A PLD featuring a general structure that allows very high logic capacity. Whereas CPLDs feature logic resources with a wide number of inputs (AND planes), FPGAs offer more narrow logic resources. FPGAs also offer a higher ratio of flip-flops to logic resources than do CPLDs.

## **Logic Block**

A relatively small circuit block that is replicated in an array in an FPD. When a circuit is implemented in an FPD, it is first decomposed into smaller sub-circuits that can each be mapped into a logic block. The term logic block is mostly used in the context of FPGAs, but it could also refer to a block of circuitry in a CPLD.


Table

11.11

PLD


Terminology



 


(a) Layout for 3-input  
2-output PLA


## Programmable Logic Array

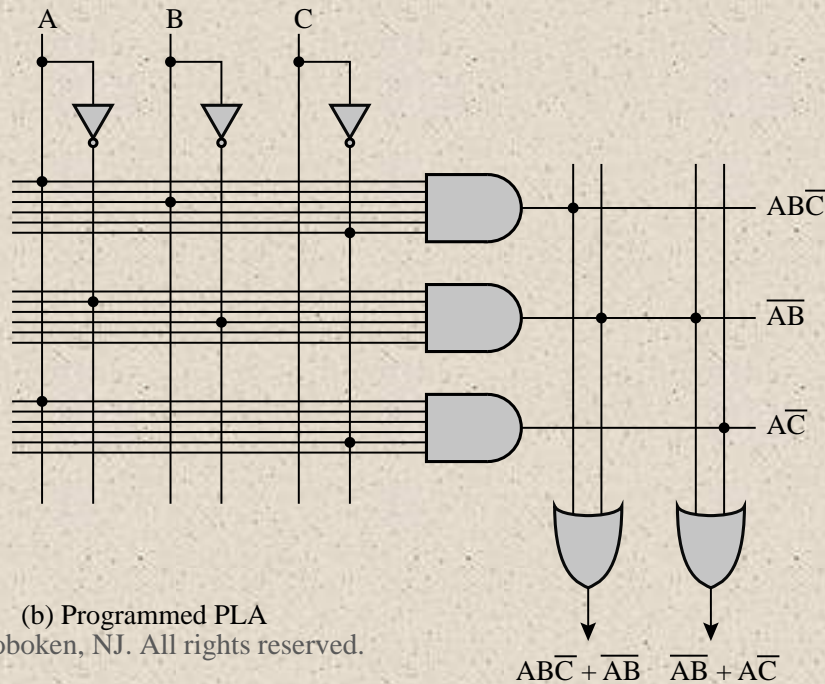

(b) Programmed PLA



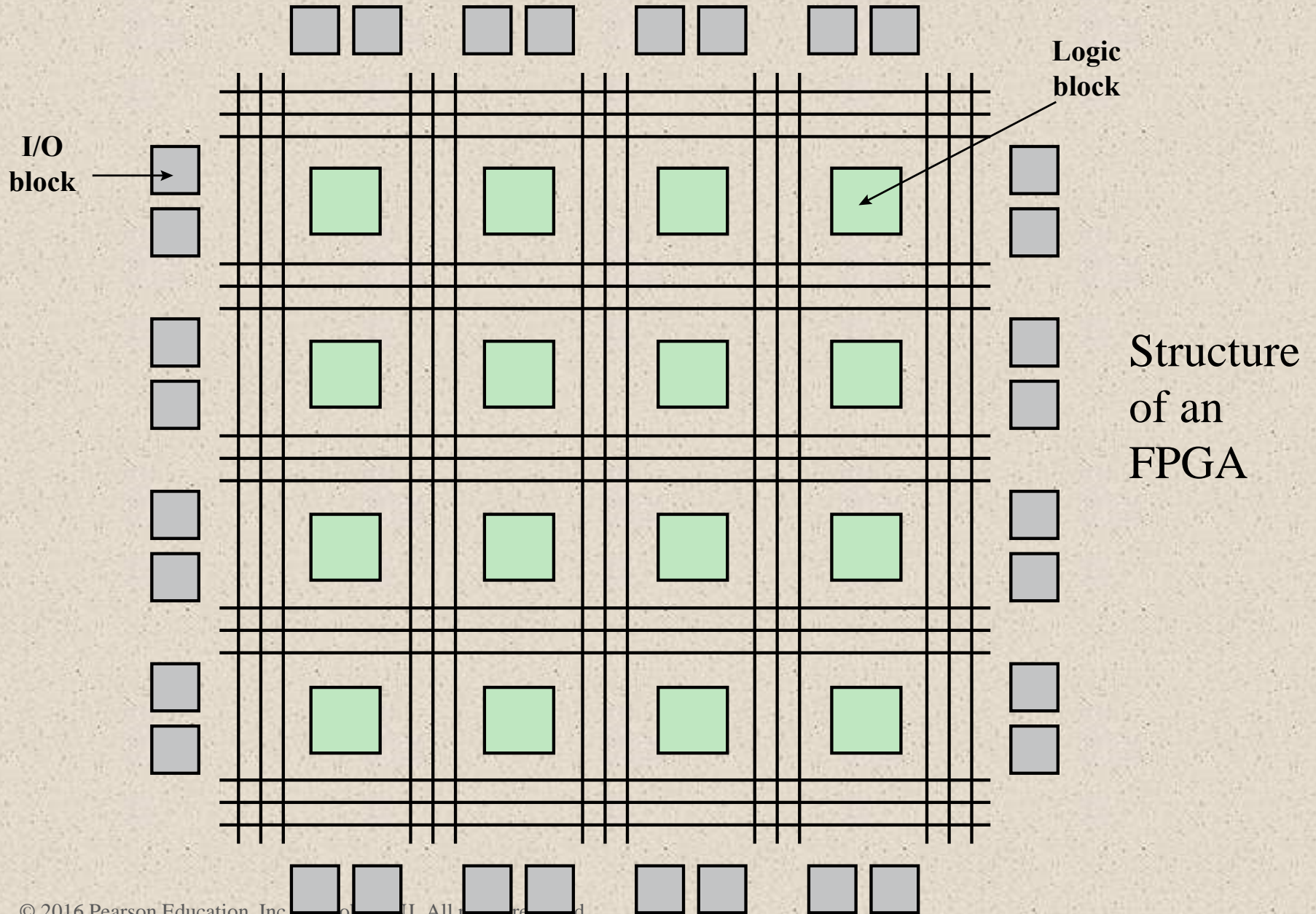

 

A Simple FPFA logic block



# Summary

## Chapter 11

- **Sequential Circuits**
  - Flip-Flops
  - Registers
  - Counters
- **Programmable Logic Devices**
  - Programmable Logic Array
  - Field-Programmable Gate Array

- Boolean Algebra
- Gates
- **Combinational Circuits**
  - Implementation of Boolean Functions
  - Multiplexers
  - Decoders
  - Read-Only-Memory
  - Adders